INDEX

Application Notes and Technical Papers

(Arranged Numerically and Categorically)

APPLICATION NOTES

APP-4	Voltage Ratings for Double-Diffused Silicon Switching Transistors — Victor H. Grinich
APP-41	Stable Wideband Emitter Followers — Paul J. Beńeteáu
APP-49	The Design of High-Speed All-Transistor Logic Circuits — Robert Foglesong
APP-51	Push-Pull Class AB Transformerless Power Amplifiers — Larry Blaser and Heitor Franco
APP-53	Measurement of the Thermal Resistance and Thermal Response of Diffused Silicon Transistors — Harold Grutchfield
APP-55	FM Multiplex Tuner Using Silicon Transistors — Larry Blaser
APP-60	DC Amplifiers Using Transistors — Paul Beńeteáu and B. Murari
APP-61	Long Delay Transistor Timer — P. Alderisio
APP-62	Silicon Transistor UHF Tuner — Thomas B. Mills
APP-63	A 6.5 Watt Auto Radio Amplifier with Direct Coupling — Jack MacIntosh
APP-64	Application of Milliwatt Micrologic® Elements — H. T. Chua
APP-67	Video Amplifier Design for Transistor TV Receivers — Samuel Schwartz
APP-68	Audio Amplifier for a Television Receiver — Samuel Schwartz
APP-69	Keyed Automatic Gain Control Circuit for TV Receivers — Samuel Schwartz
APP-70	Sync Separator Design for Transistor TV Receivers — Samuel Schwartz
APP-73	Intercarrier Sound Amplifier-Limiter and Discriminator Design for Transistor TV Receivers — Samuel Schwartz
APP-75	Stereo Tape Recorder Using Silicon Transistors — Larry Blaser
APP-76	A Transistor Video Amplifier for Radar Display — Samuel Schwartz
APP-77	Transistor Range Marker and Sweep Generator for Radar Display — Samuel Schwartz
APP-78	I-F Amplifier for a Radar Receiver — Samuel Schwartz
APP-80	Transistor Power Supply for a Portable Radar — Samuel Schwartz
APP-81	The Complete X-Band Navigational Radar Set — W. O. Hamlin
APP-84	Short-Circuit Protection in a 25-Watt Amplifier — Larry Blaser
APP-85	Micrologic® Shift Counters — George Powers
APP-88	Medium Power Silicon Transistor DC to DC Converters — Thomas B. Mills
APP-93	Transient Response Characteristics of Phototransistors — George T. Daughters
APP-103	Applications of the Silicon Planar* Field-Effect Transistor — Larry Blaser and John MacDougall
APP-105	A Monolithic Operational Amplifier — Robert Widlar
APP-106	Using Fairchild Integrated Circuits as Monostable Multivibrators — Roberts Ricks

*Planar is a patented Fairchild Process.

APP-107 Diode Transistor Micrologic® – George Powers

APP-108 The Use of Silicon Transistors in Broadcast Receivers – David Duncan

APP-109 Applications of the Silicon Planar* II MOS FET – John MacDougall

APP-111 The Improved μA702 Wideband DC Amplifier – Robert Widlar

APP-112 The Measurement of Transistor Small-Signal Y Parameters – G. Faini, G. Rescio, and G. Riva

APP-114 μA702 Circuit Design Ideas – (Six Authors)

APP-115 Maximum Integrated Circuit Utilization Through Mixing Compatible Logic Families – Robert Ricks

APP-116 The Operation and Use of a Fast Integrated Circuit Comparator – Robert Widlar

APP-117 Frequency Compensation Techniques for an Integrated Operational Amplifier – James Giles

APP-118 Counter Micrologic® A New Dimension in Multi-Function Integrated Circuits – George Powers

APP-119 Ways to Increase Speed in Large Count Binary Counters – Jack Irwin

APP-120 Using the J-K Flip-Flop in Small Modulo Counters – Jack Irwin

APP-121 A High-Efficiency Power Supply Using Micrologic® Integrated Circuits – Samuel Schwartz

APP-123 Core Memory Sense Amplifier Designs Using an Integrated Dual Comparator – Robert Widlar

APP-124 Designing with Off-the-Shelf Linear Microcircuits – Robert Widlar and James Giles

APP-125 A Versatile Tester for Linear Integrated Circuits – James Giles

APP-127 Active Filters – Donald C. Mitchell and José Herrero

TECHNICAL PAPERS

TP-24 Overloading and Spurious Responses in Transistor FM Tuners – Earl Cummins

TP-27 Forward AGC Design Considerations in Transistorized Television Receivers – Harry Suzuki

TP-28 Measurement of Transistor High-Frequency Current Gain – Heitor Franco

TP-30 Chromatron TV Color Processing Using Semiconductor Circuits – Larry Blaser and Derek Bray

TP-31 An FM Tuner Using MOS-FET's and Integrated Circuits – John Barrett, Larry Blaser, and Harry Suzuki

TP-32 A Unique Circuit Design for a High-Performance, Operational Amplifier Especially Suited to Monolithic Construction – Robert Widlar

TP-33 Some Circuit Design Techniques for Linear Integrated Circuits – Robert Widlar

TP-34 A Transistorized Chromatron Color Television Receiver – H. Ebenhoech, J. MacDougall, T. B. Mills, S. Schwartz, and H. Suzuki

TP-35 A Black and White and Color TV Video I-F Output Transistor – Derek Bray and Philip Froess

TP-36 A Low Noise, AGC Silicon Transistor Useful from LF to UHF – David Bingham, Harry Suzuki, and Charles Watson

CATEGORIC LISTING

AUDIO AND BROADCAST RECEIVER

APP-51	General	Push-Pull Class AB Transformerless Power Amplifiers	Larry Blaser and Heitor Franco
APP-63	SE1002, SE6001, 2N174	A 6.5 Watt Auto Radio Amplifier with Direct Coupling	Jack MacIntosh
APP-75	2N3565, SE7005, SE8001	Stereo Tape Recorder Using Silicon Transistors	Larry Blaser
APP-84	General	Short-Circuit Protection in a 25-Watt Amplifier	Larry Blaser
APP-108	General	The Use of Silicon Transistors in Broadcast Receivers	David Duncan
TP-24	FD7, FD100	Overloading and Spurious Responses in Transistor FM Tuners	Earl Cummins
TP-31	SE5021, SE5022	An FM Tuner Using MOS-FET's and Integrated Circuits	John Barrett, et al

CHARACTERISTICS

APP-4	2N696, 2N697	Voltage Ratings for Double-Diffused Silicon Switching Transistors	Victor H. Grinich
APP-53	General	Measurement of the Thermal Resistance and Thermal Response of Diffused Silicon Transistors	Harold Grutchfield
APP-93	1N3734, 2N986, 2N2452	Transient Response Characteristics	George T. Daughters
APP-112	2N1613, 2N2303, 2N916	The Measurement of Transistor Small-Signal Y Parameters	G. Faini, et al

COMPUTER

APP-49	2N709, 2N2368, 2N2369	The Design of High-Speed All-Transistor Logic Circuits	Robert Foglesong
APP-64	Low-Power RTuL Family	Application of Milliwatt Micrologic® Elements	H. T. Chua
APP-85	RTµL9923, 9926; DTµL9945, 9948	Micrologic® Shift Counters	George Powers
APP-106	RTµL9900, 9914; Low-Power RTµL9909, 9910	Using Fairchild Integrated Circuits as Monostable Multivibrators	Robert Ricks
APP-107	DTµL Family	Diode Transistor Micrologic®	George Powers
APP-115	RTµL and Low-Power RTµL Families	Maximum Integrated Circuit Utilization Through Mixing Compatible Logic Families	Robert Ricks
APP-119	RTµL9923	Ways to Increase Speed in Large Count Binary Counters	Jack Irwin
APP-120	Mixers	Using the J-K Flip-Flop in Small Modulo Counters	Jack Irwin

INSTRUMENT

APP-41	2N175, 2N917	Stable Wideband Emitter Followers	Paul J. Beneteau
APP-60	2N1613	DC Amplifiers Using Transistors	Paul Beneteau and B. Murari
APP-61	General	Long Delay Transistor Timer	P. Alderisio
APP-118	CμL9958, 9959, 9960	Counting Micrologic® – A New Dimension in Multi-Function Integrated Circuits	George Powers

LINEAR INTEGRATED CIRCUITS

APP-105	μA702	A Monolithic Operational Amplifier	Robert Widlar
APP-111	μA702A	The Improved μA702 Wideband DC Amplifier	Robert Widlar
APP-114	μA702	μA702 Circuit Design Ideas	(six authors)
APP-116	μA710, 711	The Operation and Use of a Fast Integrated Circuit Comparator	Robert Widlar
APP-117	μA702A	Frequency Compensation Techniques for an Integrated Operational Amplifier	James Giles
APP-123	μA711	Core Memory Sense Amplifier Designs Using an Integrated Dual Comparator	Robert Widlar
APP-124	μA702A, 709, 710, 711	Designing with Off-the-Shelf Linear Microcircuits	Robert Widlar and James Giles
APP-125	μA702A, 709, 710, 711	A Versatile Tester for Linear Integrated Circuits	James Giles
TP-32	μA709	A Unique Circuit Design for a High-Performance, Operational Amplifier Especially Suited to Monolithic Construction	Robert Widlar
TP-33	General	Some Circuit Design Techniques for Linear Integrated Circuits	Robert Widlar

RADAR

APP-76	2N2443, 2N915	A Transistor Video Amplifier for Radar Display	Samuel Schwartz
APP-77	2N2297, 2N2369, 2N2893	Transistor Range Marker and Sweep Generator for Radar Display	Samuel Schwartz
APP-78	2N918	I-F Amplifier for a Radar Receiver	Samuel Schwartz
APP-80	2N1613, 2N1893, 2N2892, 2N915	Transistor Power Supply for a Portable Radar	Samuel Schwartz
APP-81	2N2297, 2N2369, 2N2893, 2N918	The Complete X-Band Navigational Radar Set	Samuel Schwartz

VIDEO TO VHF

APP-55	2N3563	FM Multiplex Tuner Using Silicon Transistors	Larry Blaser
APP-62	SE3002, 1N82A	Silicon Transistor UHF Tuner	Thomas B. Mills
APP-67	S5310E	Video Amplifier Design for Transistor TV Receivers	Samuel Schwartz
APP-68	S5306E	Audio Amplifier for a Television Receiver	Samuel Schwartz
APP-69	SE1002	Keyed Automatic Gain Control Circuit for TV Receivers	Samuel Schwartz
APP-70	SE1001	Sync Separator Design for Transistor TV Receivers	Samuel Schwartz
APP-73	SE1001, SE3001	Intercarrier Sound Amplifier-Limiter and Discriminator Design for Transistor TV Receivers.	Samuel Schwartz
TP-27	SE5001, SE5002, SE5003	Forward AGC Design Considerations in Transistorized Television Receivers	Harry Suzuki
TP-30	General	Chromatron TV Color Processing Using Semiconductor Circuits	Larry Blaser and Derek Bray
TP-34	SE5023, SE5024, S1763	A Transistorized Chromatron Color Television Receiver	H. Ebenhoech, et al
TP-35	SE5025, 0063	A Black and White and Color TV Video I-F Output Transistor	Derek Bray and Philip Froess
TP-36	0045	A Low Noise, AGC Silicon Transistor Useful from LF to UHF	David Bingham, et al

MISCELLANEOUS

TP-28	General	Measurement of Transistor High-Frequency Current Gain	Heitor Franco
APP-88	2N2891, 2N2892,	Medium Power Silicon Transistor DC to DC Converters	Thomas B. Mills
APP-103	2N3277, 2N3278	Applications of the Silicon Planar* Field-Effect Transistor	Larry Blaser and John MacDougall
APP-109	FI100	Applications of the Silicon Planar II MOS FET	John MacDougall
APP-121	μA702A; RTμL9914, 9923, 9927	A High-Efficiency Power Supply Using Micrologic® Integrated Circuits	Samuel Schwartz
APP-127	Active Filters	Active Filters	Donald C. Mitchell and José Herrero

NOTE: All Application Notes referring to integrated circuits appear only in Microcircuit Binder; those referring to consumer applications appear only in the Consumer Products Binder. These Application Notes are available upon request.

*Planar is a patented Fairchild process.